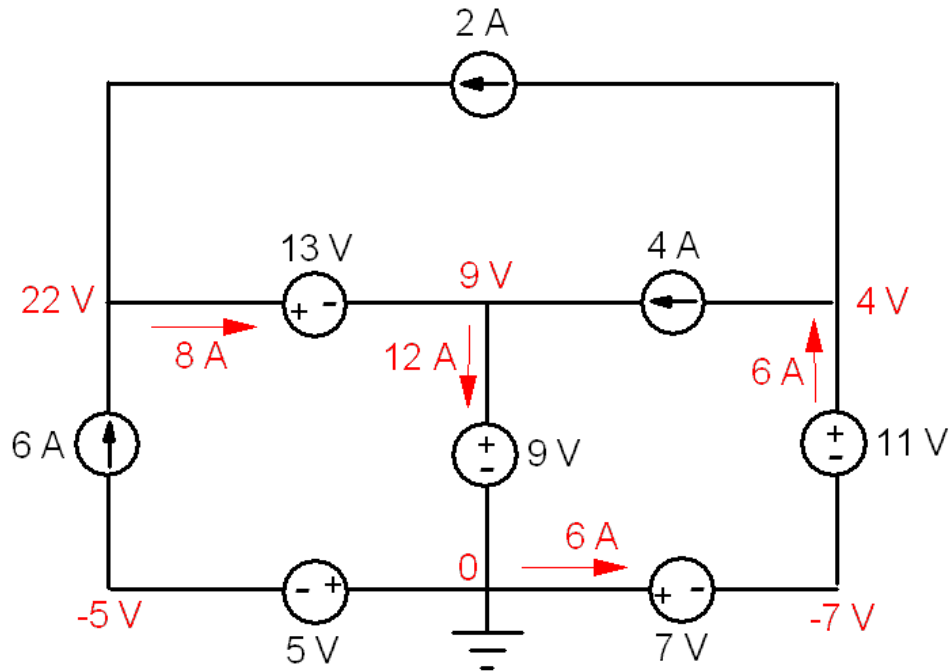


(3 problems, 10 pts each)

1. For the circuit below, calculate the power supplied or absorbed (specify one) by each of the eight sources.



Solution:


Apply KCL and KVL to come up with all the voltages and currents as shown in red.

- | | | |
|------------------------|----------|--------------------------------------|
| • 2 A current source: | Supplies | $2 \times (22 - 4) = 36 \text{ W.}$ |
| • 4A current source: | Supplies | $4 \times (9 - 4) = 20 \text{ W.}$ |
| • 6A current source: | Supplies | $6 \times (22 + 5) = 162 \text{ W.}$ |
| • 5 V voltage source: | Absorbs | $5 \times 6 = 30 \text{ W.}$ |
| • 7 V voltage source: | Absorbs | $7 \times 6 = 42 \text{ W.}$ |
| • 9 V voltage source: | Absorbs | $9 \times 12 = 108 \text{ W.}$ |
| • 11 V voltage source: | Supplies | $11 \times 6 = 66 \text{ W.}$ |
| • 13 V voltage source: | Absorbs | $13 \times 8 = 104 \text{ W.}$ |

Total power absorbed = $30 + 42 + 108 + 104 = 284 \text{ W}$.

Total power supplied = $36 + 20 + 162 + 66 = 284 \text{ W}.$

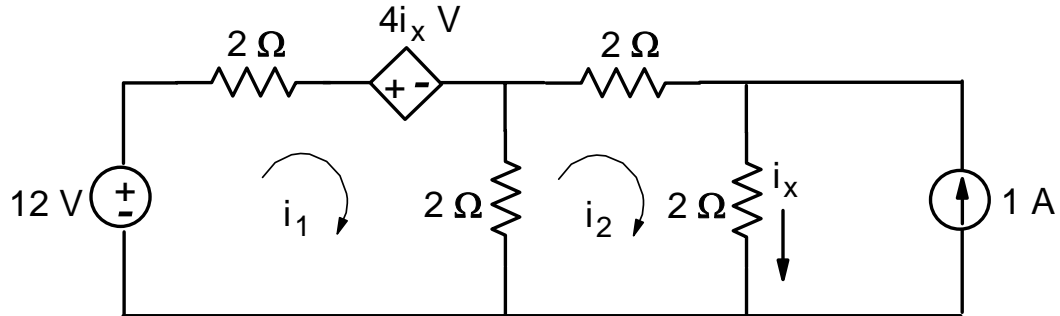2. Solve the circuit below for i_1 , i_2 , i_x .



Solution:

$$i_x = i_2 + 1$$

KVL, left loop,

$$12 - 2 i_1 - 4 i_x - 2 (i_1 - i_2) = 0$$

KVL, middle loop,

$$2 (i_1 - i_2) - 2 i_2 - 2 i_x = 0$$

Eliminate i_x from the above eqs.,

$$4 - 2 i_1 - i_2 = 0$$

$$i_1 - 3 i_2 - 1 = 0$$


Solve

$$i_1 = 13/7 \text{ A}$$

$$i_2 = 2/7 \text{ A}$$


$$i_x = 9/7 \text{ A.}$$

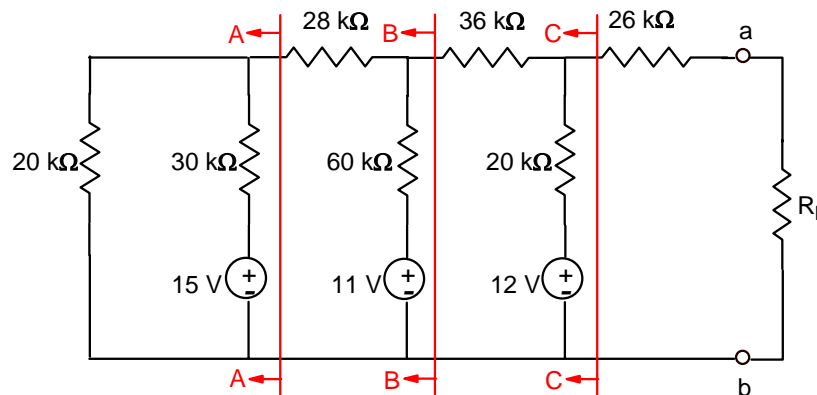3. Find the value of R_L across port (a,b) that maximizes the power absorbed in R_L . How much is the maximum power absorbed?



Solution: Apply Thevenin's theorem repeatedly,


AA:

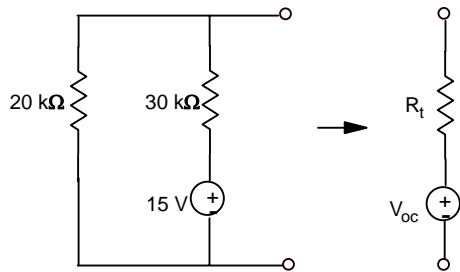

$$R_t = 20\text{k} // 30\text{k} = 12\text{k},$$

$$V_{oc} = 15 \times 20\text{k} / (20\text{k} + 30\text{k}) = 6\text{ V}.$$


BB:

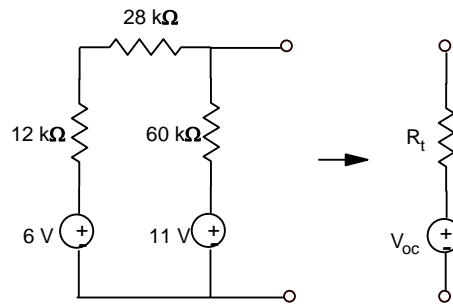

$$R_t = (12\text{k} + 28\text{k}) // 60\text{k} = 24\text{k},$$

$$V_{oc} = 11 - 60\text{k} \times (11 - 6) / (40\text{k} + 60\text{k}) = 8\text{ V}.$$


CC:

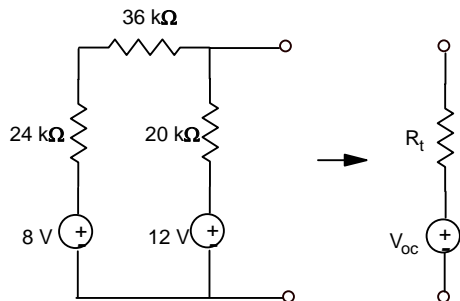

$$R_t = (24\text{k} + 36\text{k}) // 20\text{k} = 15\text{k},$$

$$V_{oc} = 12 - 20\text{k} \times (12 - 8) / (60\text{k} + 20\text{k}) = 11\text{ V}.$$

Final circuit:

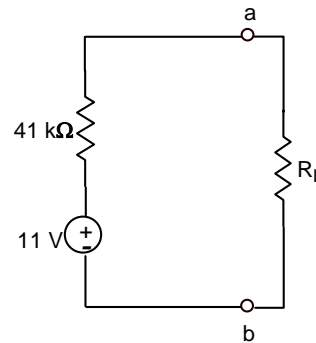

For maximum power, $R_L = 41\text{ k}\Omega$.
Maximum power = $11^2 / (4 \times 41\text{k}) = 121/164\text{ mW}$.