

ECE 35 Homework #7 (Spring 2023, Taur)

All homework problems come from the textbook, "Introduction to Electric Circuits", by Svoboda & Dorf, 9th Edition.

P 8.3-3 The circuit shown in Figure P 8.3-3 is at steady state before the switch closes at time $t = 0$. Determine the capacitor voltage, $v(t)$, for $t > 0$.

Answer: $v(t) = -6 + 18e^{-6.67t}$ V for $t > 0$



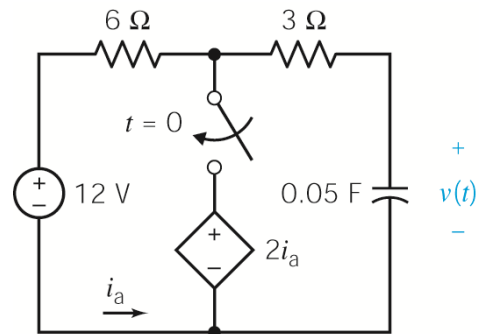
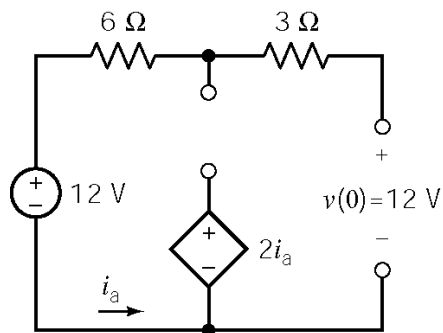


Figure P 8.3-3

Solution: Before the switch closes:

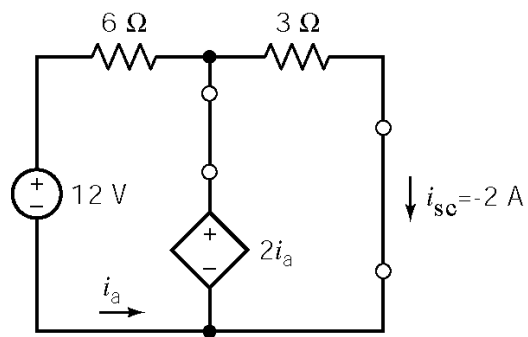

After the switch closes:

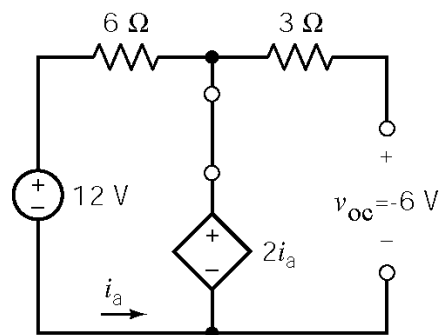

Therefore $R_t = \frac{-6}{-2} = 3 \Omega$ so $\tau = 3(0.05) = 0.15 \text{ s}$

Finally,

$$v(t) = v_{oc} + (v(0) - v_{oc}) e^{-t/\tau} = -6 + 18 e^{-6.67t} \text{ V for } t > 0$$

P 8.3-10 A security alarm for an office building door is modeled by the circuit of Figure P 8.3-10. The switch represents the door interlock, and v is the alarm indicator voltage. Find $v(t)$ for $t > 0$ for the circuit of Figure P 8.3-10. The switch has been closed for a long time at $t = 0^-$.



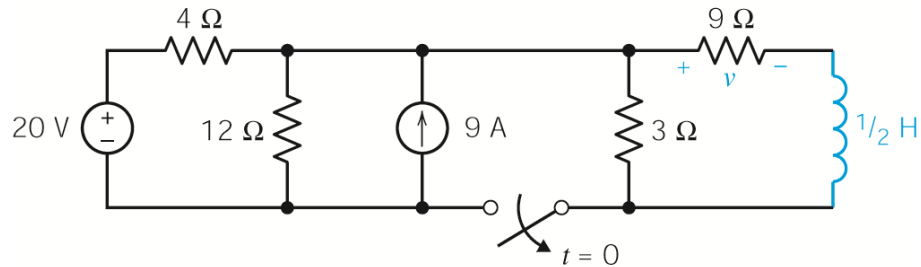


Figure P 8.3-10

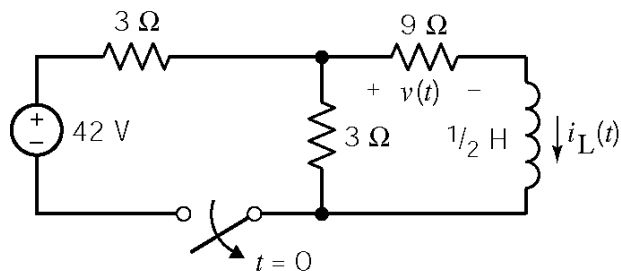
Solution: First, use source transformations to obtain the equivalent circuit



for $t < 0$:

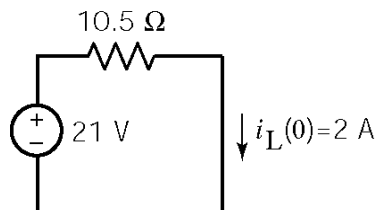

for $t > 0$:

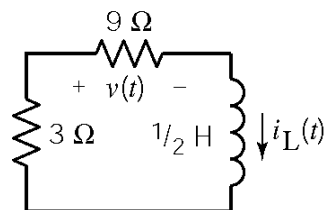

$$\text{So } i_L(0) = 2 \text{ A}, I_{sc} = 0, R_t = 3 + 9 = 12 \Omega, \tau = \frac{L}{R_t} = \frac{1/2}{12} = \frac{1}{24} \text{ s}$$

$$\text{and } i_L(t) = 2e^{-24t} \quad t > 0$$

$$\text{Finally } v(t) = 9 i_L(t) = 18 e^{-24t} \quad t > 0$$

P 8.3-13 The circuit shown in Figure P 8.3-13 is at steady state when the switch opens at time $t = 0$. Determine $v(t)$ for $t \geq 0$.


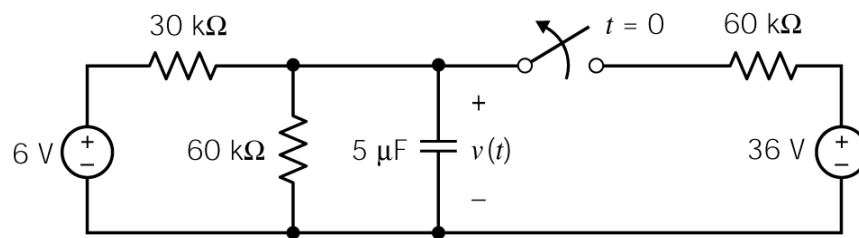


Figure P 8.3-13

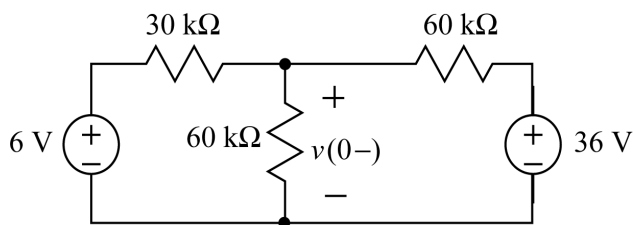Solution: Before $t = 0$, with the switch closed and the circuit at the steady state, the capacitor acts like an open circuit so we have




Using superposition

$$v(0-) = \frac{60 \cancel{30}}{30 + (60 \cancel{30})} 6 + \frac{60 \cancel{30}}{60 + (60 \cancel{30})} 36 = \left(\frac{1}{2}\right) 6 + \left(\frac{1}{4}\right) 36 = 12 \text{ V}$$

The capacitor voltage is continuous so $v(0+) = v(0-) = 12 \text{ V}$.

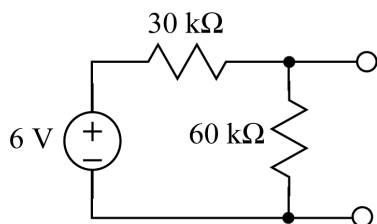After $t = 0$ the switch is open. Determine the Thevenin equivalent circuit for the part of the circuit connected to the capacitor:



$$v_{oc} = \frac{60}{60 + 30} 6 = 4 \text{ V}$$

$$R_t = 30 \cancel{30} = 20 \text{ k}\Omega$$

The time constant is $\tau = R_t C = (20 \times 10^3)(5 \times 10^{-6}) = 0.1 \text{ s}$ so $\frac{1}{\tau} = 10 \frac{1}{\text{s}}$.

The capacitor voltage is given by

$$v(t) = (v(0+) - v_{oc})e^{-t/\tau} + v_{oc} = (12 - 4)e^{-10t} + 4 = 4 + 8e^{-10t} \text{ V for } t \geq 0$$

P 8.3-14 The circuit shown in Figure P 8.3-14 is at steady state when the switch closes at time $t = 0$. Determine $i(t)$ for $t \geq 0$.


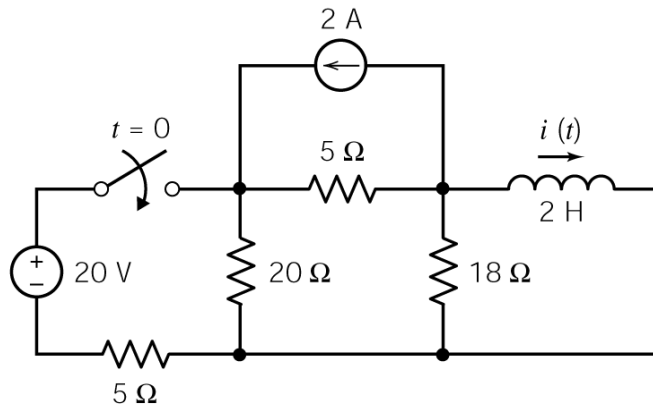



Figure P 8.3-14

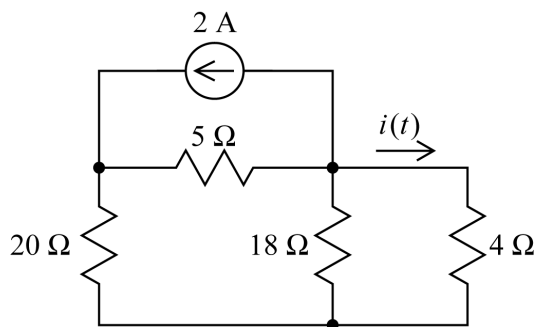Solution: Before $t = 0$, with the switch open and the circuit at steady state, the inductor acts like a short circuit so we have




$$i(t) = -\frac{18}{4+18} \left[\frac{5}{5+20+(18 \parallel 4)} 2 \right] = 0.29 \text{ A}$$

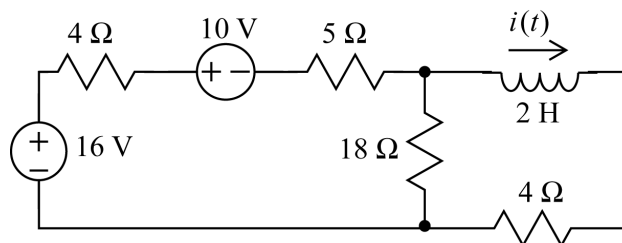After $t = 0$, we can replace the part of the circuit connected to the inductor by its Norton equivalent circuit. First, performing a couple of source transformations reduces the circuit to



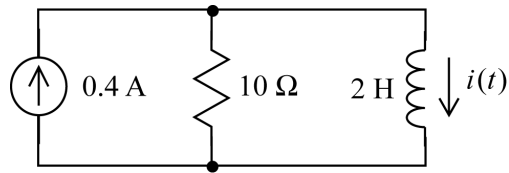Next, replace the series voltage sources by an equivalent voltage source, replace the series resistors by an equivalent resistor and do a couple of source transformations to get



$$\tau = \frac{2}{10} = 0.25 \quad \Rightarrow \quad \frac{1}{\tau} = 5 \frac{1}{s}$$

so

The current is given by $i(t) = [0.29 - 0.4]e^{-5t} + 0.4 = 0.4 - 0.11e^{-5t} \text{ A for } t \geq 0$

P 8.3-19 The circuit shown in Figure P 8.3-19 is at steady state before the switch closes. Find $v(t)$ for $t \geq 0$.


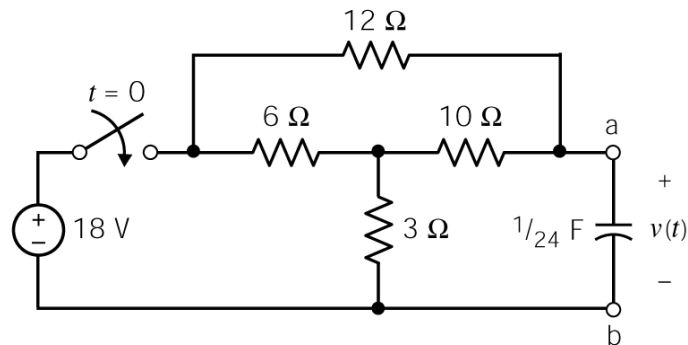


Figure P 8.3-19

Solution: Before the switch closes $v(t) = 0$ so $v(0+) = v(0-) = 0 \text{ V}$.

For $t > 0$, we find the Thevenin equivalent circuit for the part of the circuit connected to the capacitor, i.e. the part of the circuit to the left of the terminals $a - b$.

Write mesh equations to find v_{oc} :

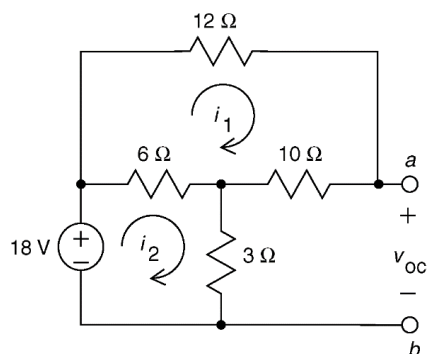

Mesh equations:

$$12 i_1 + 10 i_1 - 6 (i_2 - i_1) = 0$$

$$6 (i_2 - i_1) + 3 i_2 - 18 = 0$$


$$28 i_1 = 6 i_2$$

$$9 i_2 - 6 i_1 = 18$$

$$v_{oc} = 3 i_2 + 10 i_1 = 3 \left(\frac{7}{3} \right) + 10 \left(\frac{1}{2} \right) = 12 \text{ V}$$

Using KVL,

Find R_t :

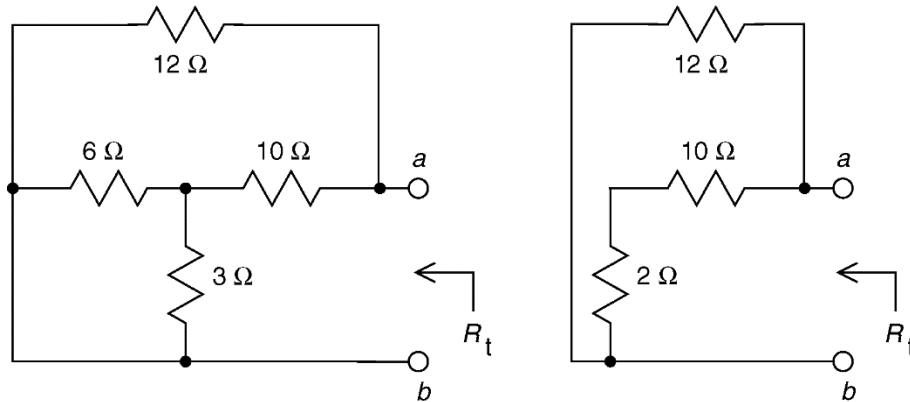

$$R_t = \frac{12(10+2)}{12+(10+2)} = 6 \Omega$$

Then

$$\tau = R_t C = 6 \left(\frac{1}{24} \right) = \frac{1}{4} \text{ s} \quad \Rightarrow \quad \frac{1}{\tau} = 4 \frac{1}{\text{s}}$$

and

$$v(t) = (v(0+) - v_{oc}) e^{-t/\tau} + v_{oc} = (0 - 12) e^{-4t} + 12 = 12(1 - e^{-4t}) \text{ V for } t \geq 0$$

P 8.3-20 The circuit shown in Figure P 8.3-20 is at steady state before the switch closes. Determine $i(t)$ for $t \geq 0$.


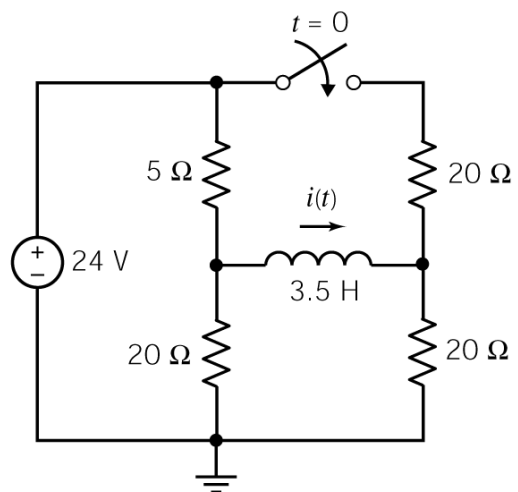


Figure P 8.3-20

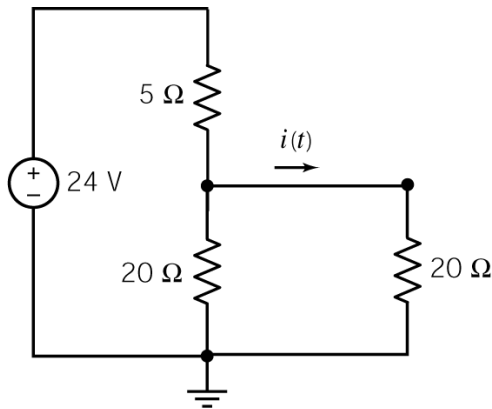Solution: Before the switch closes the circuit is at steady state so the inductor acts like a short circuit. We have




$$i(t) = \frac{1}{2} \left(\frac{24}{5 + (20 \parallel 20)} \right) = 0.8 \text{ A}$$

so


$$i(0+) = i(0-) = 0.8 \text{ A}$$

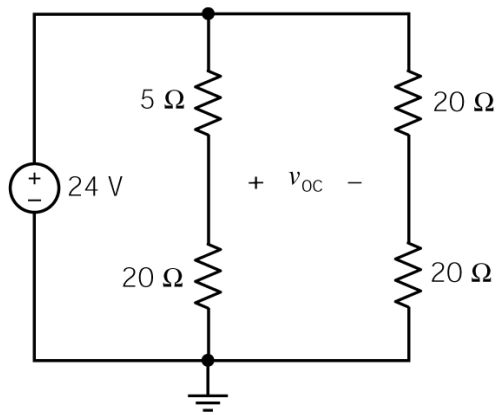After the switch closes, find the Thevenin equivalent circuit for the part of the circuit connected to the inductor.



Using voltage division twice
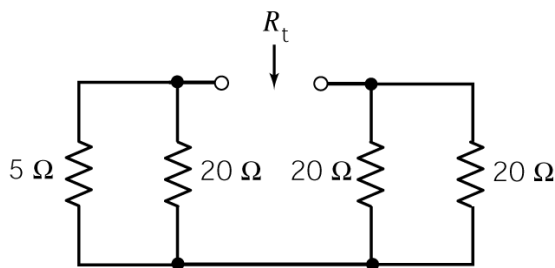
$$v_{oc} = \left(\frac{20}{25} - \frac{1}{2} \right) 24 = 7.2 \text{ V}$$



$$R_t = (5 \parallel 20) + (20 \parallel (20 \parallel 20)) = 14 \Omega$$

$$i_{sc} = \frac{v_{oc}}{R_t} = \frac{7.2}{14} = 0.514 \text{ A}$$

Then

$$\tau = \frac{L}{R_t} = \frac{3.5}{14} = \frac{1}{4} \text{ s} \quad \Rightarrow \quad \frac{1}{\tau} = 4 \frac{1}{\text{s}}$$

and

$$i(t) = (i(0+) - i_{sc})e^{-t/\tau} + i_{sc} = (0.8 - 0.514)e^{-4t} + 0.514 = 0.286e^{-4t} + 0.514 \text{ A for } t \geq 0$$

P 8.3-22 The circuit shown in Figure P 8.3-22 is at steady state when the switch closes at time $t = 0$. Determine $i(t)$ for $t \geq 0$.


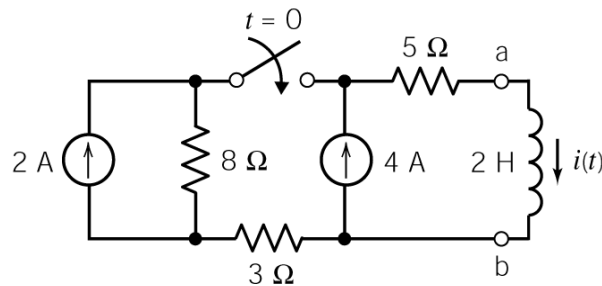



Figure P 8.3-22

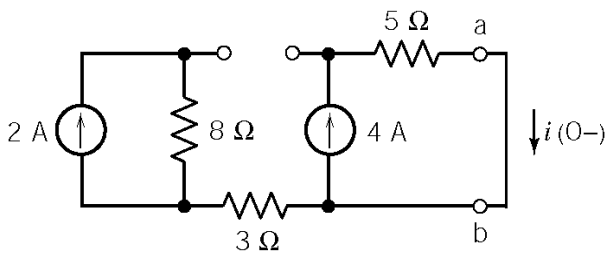Solution: Before $t = 0$, with the switch open and the circuit at steady state, the inductor acts like a short circuit so we have




$$i(0+) = i(0-) = 4 \text{ A}$$

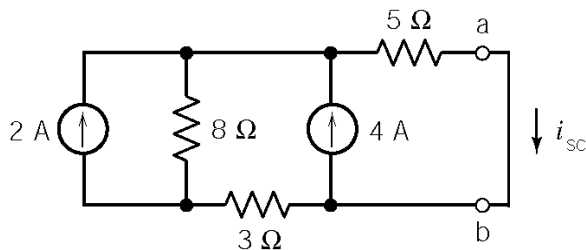After $t = 0$, we can replace the part of the circuit connected to the inductor by its Norton equivalent circuit.



Using superposition, the short circuit current is given by
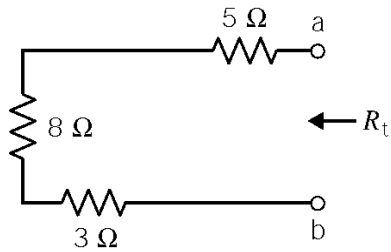
$$i_{sc} = \left(\frac{8}{8 + (5 + 3)} \right) 2 + \left(\frac{3 + 8}{(3 + 8) + 5} \right) 4 = 3.75 \text{ A}$$



$$R_t = 8 + 3 + 5 = 16 \, \Omega$$

so

$$\tau = \frac{2}{16} = 0.125 \, \text{s} \Rightarrow \frac{1}{\tau} = 8 \, \frac{1}{\text{s}}$$

The inductor current is given by

$$i_L(t) = (i(0+) - i_{sc})e^{-t/\tau} + i_{sc} = (4 - 3.75)e^{-8t} + 3.75 = 3.75 - 0.25e^{-8t} \, \text{A} \quad \text{for } t \geq 0$$

P 8.4-1 The circuit shown in Figure P 8.4-1 is at steady state before the switch closes at time $t = 0$. The switch remains closed for 1.5 s and then opens. Determine the capacitor voltage, $v(t)$, for $t > 0$.

Hint: Determine $v(t)$ when the switch is closed. Evaluate $v(t)$ at time $t = 1.5$ s to get $v(1.5)$. Use $v(1.5)$ as the initial condition to determine $v(t)$ after the switch opens again.

Answer:
$$v(t) = \begin{cases} 5 + 5e^{-0.5t} \, \text{V} & \text{for } 0 < t < 1.5 \, \text{s} \\ 10 - 2.64e^{-2.5(t-1.5)} \, \text{V} & \text{for } 1.5 \, \text{s} < t \end{cases}$$


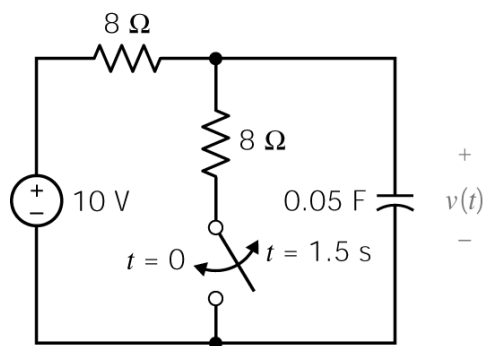


Figure P 8.4-1

Solution:

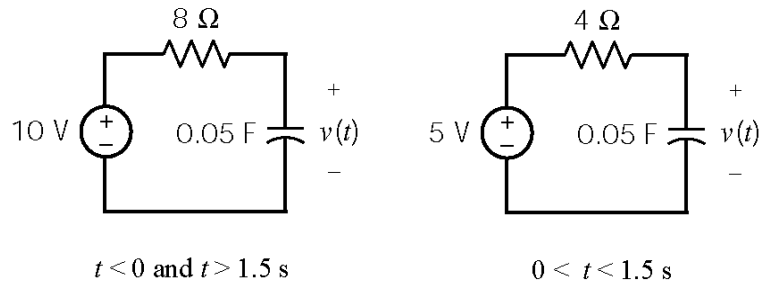Replace the part of the circuit connected to the capacitor by its Thevenin equivalent circuit to get:



Before the switch closes at $t = 0$ the circuit is at steady state so $v(0) = 10 \text{ V}$. For $0 < t < 1.5 \text{ s}$, $v_{oc} = 5 \text{ V}$ and $R_t = 4 \Omega$ so $\tau = 4 \times 0.05 = 0.2 \text{ s}$. Therefore

$$v(t) = v_{oc} + (v(0) - v_{oc}) e^{-t/\tau} = 5 + 5e^{-5t} \text{ V} \quad \text{for } 0 < t < 1.5 \text{ s}$$

At $t = 1.5 \text{ s}$, $v(1.5) = 5 + 5e^{-0.05(1.5)} = 5 \text{ V}$.

For $1.5 \text{ s} < t$, $v_{oc} = 10 \text{ V}$ and $R_t = 8 \Omega$ so $\tau = 8 \times 0.05 = 0.4 \text{ s}$.

Therefore


$$v(t) = v_{oc} + (v(1.5) - v_{oc}) e^{-(t-1.5)/\tau} = 10 - 5e^{-2.5(t-1.5)} \text{ V} \quad \text{for } 1.5 \text{ s} < t$$

Finally


$$v(t) = \begin{cases} 5 + 5e^{-5t} \text{ V} & \text{for } 0 < t < 1.5 \text{ s} \\ 10 - 5e^{-2.5(t-1.5)} \text{ V} & \text{for } 1.5 \text{ s} < t \end{cases}$$

P 8.4-4 An electronic flash on a camera uses

 The circuit shown in Figure P 8.4-4. Assume



Solution:

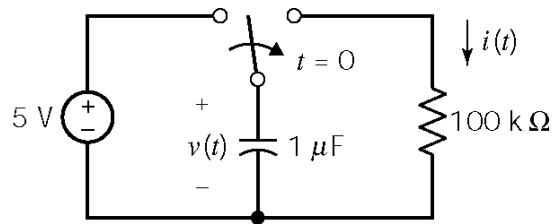

$$v(0) = 5 \text{ V}, \quad v(\infty) = 0 \quad \text{and}$$

$$\tau = 10^5 \times 10^{-6} = 0.1 \text{ s}$$

$$\therefore v(t) = 5 e^{-10t} \text{ V for } t > 0$$

$$2.5 = 5 e^{-10t_1} \quad \underline{t_1 = 0.0693 \text{ s}}$$

$$i(t_1) = \frac{v(t_1)}{100 \times 10^3} = \frac{2.5}{100 \times 10^3} = \underline{25 \text{ } \mu\text{A}}$$

P 8.6-11 The voltage source voltage in the circuit shown in Figure P 8.6-11 is

$$v_s(t) = 5 + 20u(t)$$

Determine $i(t)$ for $t \geq 0$.


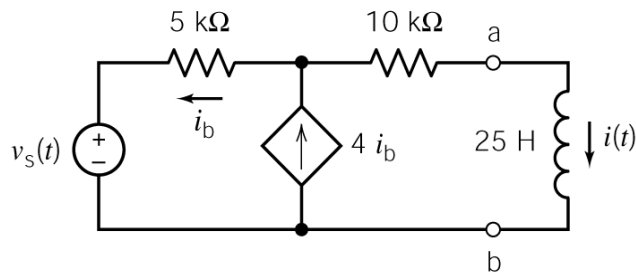


Figure P 8.6-11

Solution:

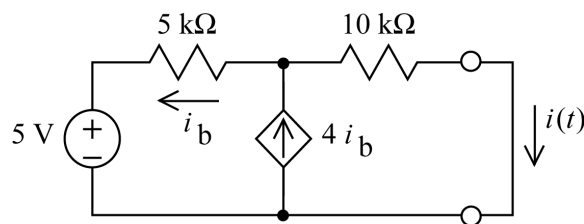For $t > 0$ the circuit is at steady state so the inductor acts like a short circuit:




Apply KVL to the supermesh corresponding to the dependent source to get

$$-5000i_b + 1000(3i_b) - 5 = 0 \quad \Rightarrow \quad i_b = 0.2 \text{ mA}$$

Apply KVL to get


$$i(t) = 3i_b = 0.6 \text{ mA}$$

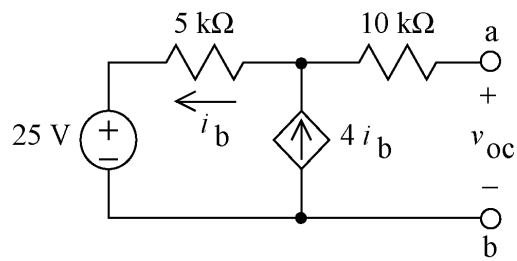For $t > 0$, find the Norton equivalent circuit for the part of the circuit that is connected to the inductor.



Apply KCL at the top node of the dependent source to see that $i_b = 0$ A. Then
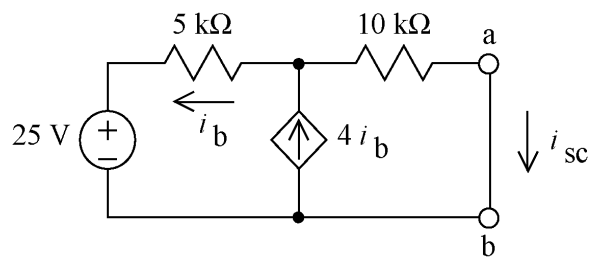
$$v_{oc} = 25 - 5000(i_b) = 25 \text{ V}$$



Apply KVL to the supermesh corresponding to the dependent source to get

$$-5000 i_b + 10000(3 i_b) - 25 = 0 \Rightarrow i_b = 1 \text{ mA}$$

Apply KCL to get

$$i_{sc} = 3 i_b = 3 \text{ mA}$$

$$R_t = \frac{v_{oc}}{i_{sc}} = 8.33 \text{ k}\Omega$$

Then

$$\tau = \frac{25}{8333} = 3 \text{ ms}$$

Then


$$\frac{1}{\tau} = 333 \frac{1}{\text{s}}$$

So

Now

$$i(t) = [0.6 - 3]e^{-333t} + 3 = 3 - 2.4e^{-333t} \text{ mA for } t \geq 0$$

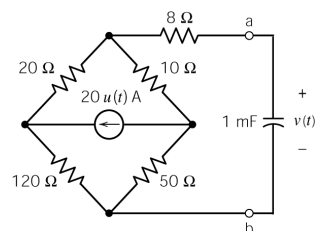
P 8.6-15 Determine $v(t)$ for $t \geq 0$ for the circuit shown in Figure P 8.6-15.




Solution:

When $t < 0$ and the circuit is at steady state, the capacitor acts like an open circuit. The 0 A current source also acts like an open circuit. The initial condition is

$$v(0+) = v(0-) = 0 \text{ V}$$

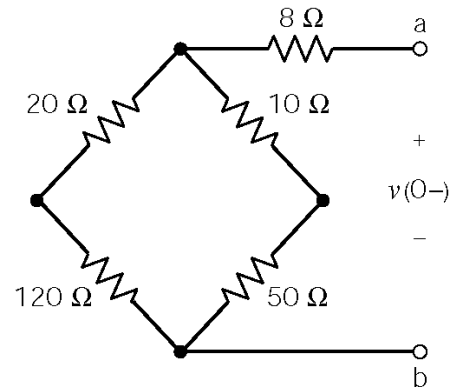

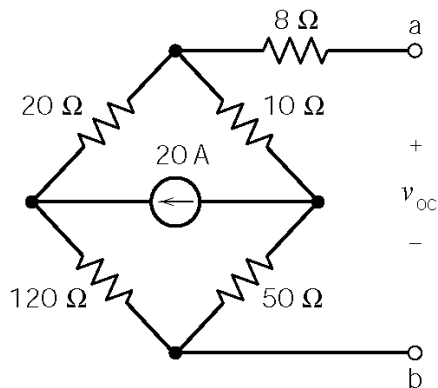
For $t \geq 0$, we find the Thevenin equivalent circuit for the part of the circuit connected to the capacitor.



$$v_{oc} = \left[\frac{170}{170+30}(20) \right] 10 - \left[\frac{30}{170+30}(20) \right] 50$$

$$= \frac{170(20)(10) - 30(20)(50)}{200} = \frac{4000}{200} = 20 \text{ V}$$
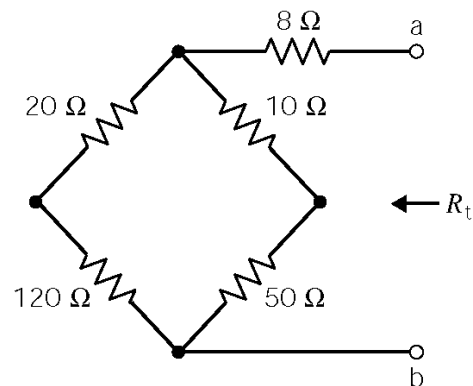
$$R_t = 8 + \frac{(20+120)(10+50)}{(20+120)+(10+50)} = 50 \text{ } \Omega$$



The time constant is $\tau = R_t C = (50)(10^{-3}) = 0.05 \text{ s}$ so $\frac{1}{\tau} = 20 \frac{1}{\text{s}}$.

The capacitor voltage is given by

$$v(t) = (v(0+) - v_{oc})e^{-t/\tau} + v_{oc} = (0 - 20)e^{-20t} + 20 = 20(1 - e^{-20t}) \text{ V for } t \geq 0$$

P8.6-19 Determine the current $i_o(t)$ in the circuit shown in Figure P8.6-19.

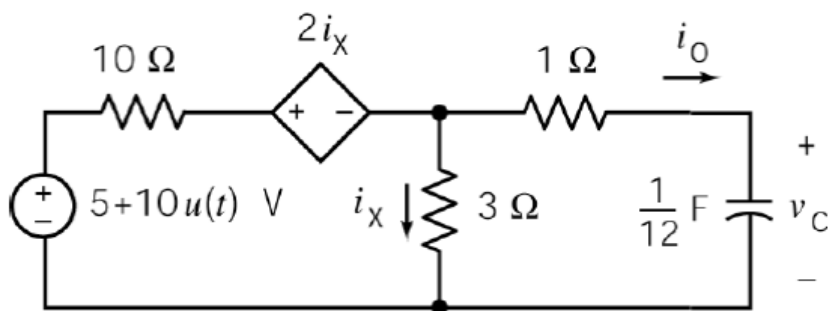


Figure P8.6-19

Solution: This is a first order circuit containing a capacitor. First, determine $v_c(t)$.

Consider the circuit for time $t < 0$.

Step 1: Determine the initial capacitor voltage.

The circuit will be at steady state before the source voltage changes abruptly at time $t = 0$.

The source voltage will be 5 V, a constant.

The capacitor will act like an open circuit.

P 8.6-23 Determine $v(t)$ for $t > 0$ for the circuit shown in Figure P 8.6-23.


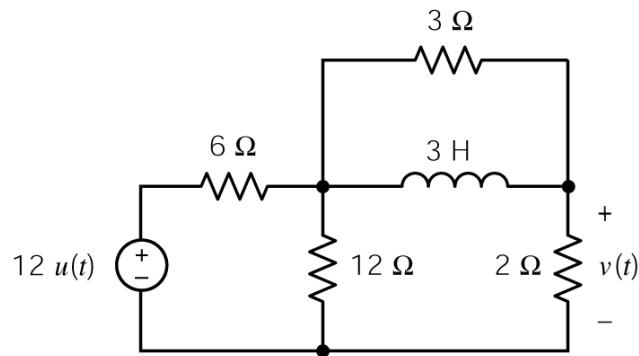
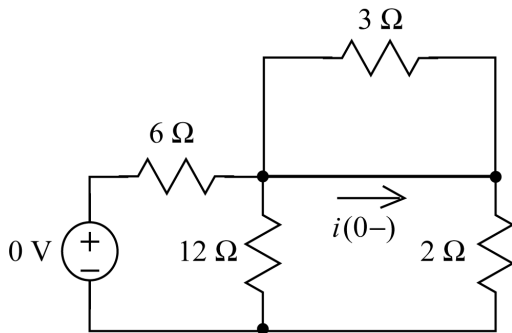


Figure P 8.6-23

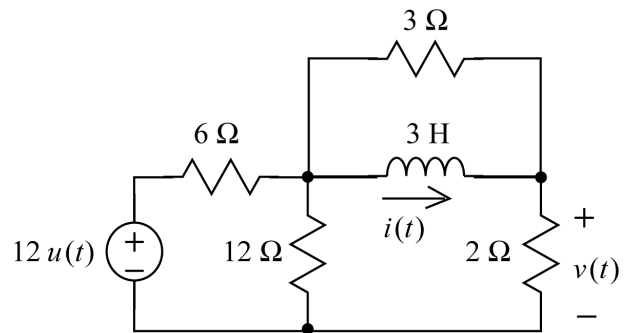Solution: The resistor voltage, $v(t)$, may not be continuous at time $t = 0$. The inductor will be continuous. We will find the inductor current first and then find $v(t)$. Label the inductor current as $i(t)$.




For $t < 0$ the circuit is at steady state and the inductor acts like a short circuit. The initial condition is

$$i(0+) = i(0-) = 0 \text{ A}$$

For $t > 0$ use source transformations to simplify the part of the circuit connected to the inductor until it is a Norton equivalent circuit.

Recognize that

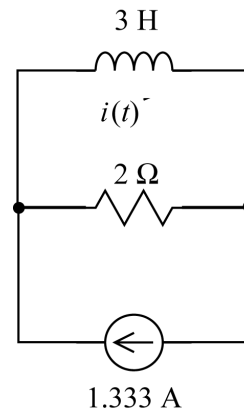

$$R_t = 2 \, \Omega \quad \text{and} \quad i_{sc} = 1.333 \, \text{A}$$

$$\tau = \frac{L}{R_t} = \frac{3}{2} \quad \Rightarrow \quad \frac{1}{\tau} = 0.667 \, \frac{1}{\text{s}}$$

The time constant is

Then
$$i(t) = (i(0+) - i_{sc})e^{-t/\tau} + i_{sc} = 1.333(1 - e^{-0.667t}) \, \text{A} \quad \text{for } t \geq 0$$

Returning to the original circuit we see that

$$\begin{aligned} \frac{v(t)}{2} &= i(t) + \frac{3 \frac{d}{dt} i(t)}{3} = i(t) + \frac{d}{dt} i(t) \\ &= 1.333(1 - e^{-0.667t}) + (-0.667)(1.333)(-e^{-0.667t}) = 1.333 - 0.4439e^{-0.667t} \end{aligned}$$

Finally
$$v(t) = 2.667 - 0.889e^{0.667t} \, \text{V} \quad \text{for } t > 0$$