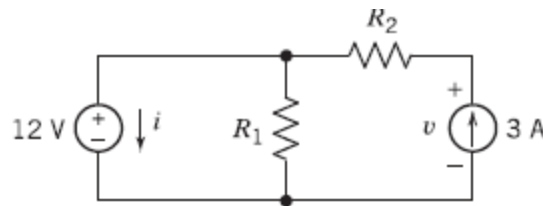


## ECE 35 Homework #2 (Spring 2023, Taur)

All homework problems come from the textbook, "Introduction to Electric Circuits", by Svoboda & Dorf, 9th Edition.


**P 3.2-3** Consider the circuit shown in Figure P 3.2-3.

- (a) Suppose that  $R_1 = 8\ \Omega$  and  $R_2 = 4\ \Omega$ . Find the current  $i$  and the voltage  $v$ .
- (b) Suppose, instead, that  $i = 2.25\ \text{A}$  and  $v = 42\ \text{V}$ . Determine the resistances  $R_1$  and  $R_2$ .
- (c) Suppose, instead, that the voltage source supplies  $24\ \text{W}$  of power and that the current source supplies  $9\ \text{W}$  of power. Determine the current  $i$ , the voltage  $v$ , and the resistances  $R_1$  and  $R_2$ .



**Figure P 3.2-3**

**Solution:**

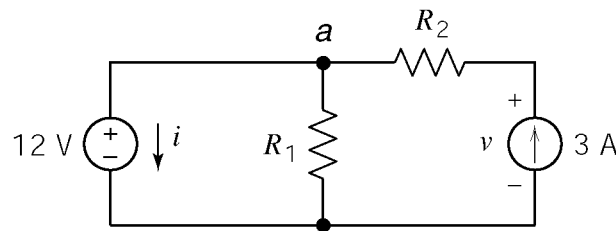

$$\text{KVL : } -12 - R_2(3) + v = 0 \quad (\text{outside loop})$$

$$v = 12 + 3R_2 \quad \text{or} \quad R_2 = \frac{v-12}{3}$$

$$\text{KCL} \quad i + \frac{12}{R_1} - 3 = 0 \quad (\text{top node})$$

$$i = 3 - \frac{12}{R_1} \quad \text{or} \quad R_1 = \frac{12}{3-i}$$

(a)  $v = 12 + 3(4) = 24 \text{ V}$  and  $i = 3 - \frac{12}{8} = 1.5 \text{ A}$

(b)  $R_2 = \frac{42-12}{3} = 10 \Omega$  ;  $R_1 = \frac{12}{3-2.25} = 16 \Omega$

(c)  $24 = -12 i$ , because 12 and  $i$  adhere to the passive convention.


$$\therefore \underline{i = -2 \text{ A}} \quad \text{and} \quad R_1 = \frac{12}{3+2} = \underline{2.4 \Omega}$$

$9 = 3v$ , because 3 and  $v$  do not adhere to the passive convention

$$\therefore \underline{v = 3 \text{ V}} \quad \text{and} \quad R_2 = \frac{3-12}{3} = \underline{-3 \Omega}$$


The situations described in (b) and (c) cannot occur if  $R_1$  and  $R_2$  are required to be nonnegative.

**P 3.2-12** Determine the voltage and current of each of the circuit elements in the circuit shown in Figure P 3.2-12.

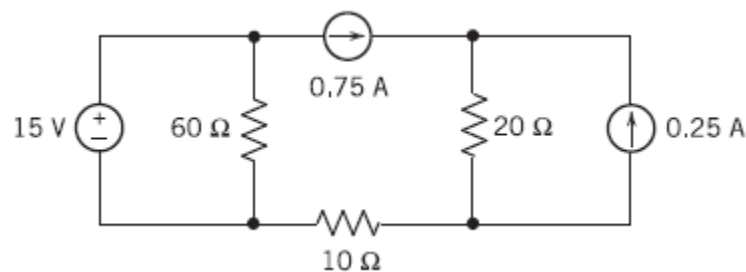

**Figure P 3.2-12**

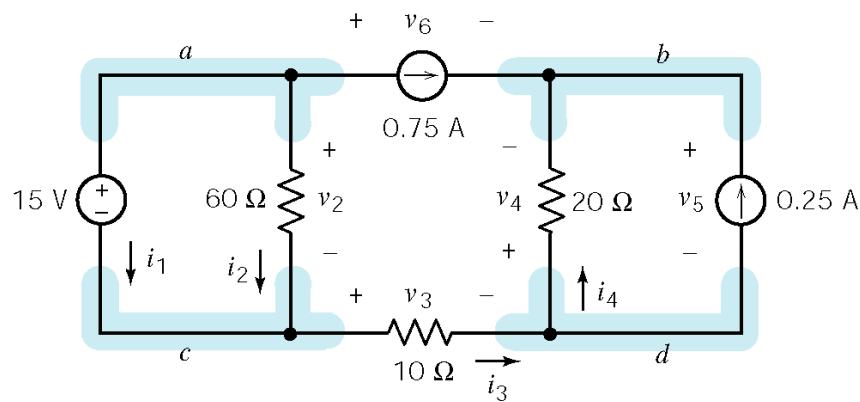**Solution:** We can label the circuit as follows:



The subscripts suggest a numbering of the circuit elements. Apply KCL at node  $b$  to get

$$i_4 + 0.25 + 0.75 = 0 \Rightarrow i_4 = -1.0 \text{ A}$$

Next, apply KCL at node  $d$  to get

$$i_3 = i_4 + 0.25 = -1.0 + 0.25 = -0.75 \text{ A}$$

Next, apply KVL to the loop consisting of the voltage source and the  $60 \Omega$  resistor to get

$$v_2 - 15 = 0 \Rightarrow v_2 = 15 \text{ V}$$

Apply Ohm's law to each of the resistors to get

$$i_2 = \frac{v_2}{60} = \frac{15}{60} = 0.25 \text{ A}, \quad v_3 = 10 i_3 = 10(-0.75) = -7.5 \text{ V}$$

and

$$v_4 = 20 i_4 = 20(-1) = -20 \text{ V}$$

Next, apply KCL at node  $c$  to get

$$i_1 + i_2 = i_3 \Rightarrow i_1 = i_3 - i_2 = -0.75 - 0.25 = -1.0 \text{ A}$$

Next, apply KVL to the loop consisting of the  $0.75 \text{ A}$  current source and three resistors to get

$$v_6 - v_4 - v_3 - v_2 = 0 \Rightarrow v_6 = v_4 + v_3 + v_2 = -20 + (-7.5) + 15 = -12.5 \text{ V}$$

Finally, apply KVL to the loop consisting of the  $0.25 \text{ A}$  current source and the  $20 \Omega$  resistor to get

$$v_5 + v_4 = 0 \Rightarrow v_5 = -v_4 = -(-20) = 20 \text{ V}$$

**P 3.2-18** Determine the value of the current  $i_m$  in Figure P 3.2-18a.

**Hint:** Apply KVL to the closed path a-b-d-c-a in Figure P 3.2-18b to determine  $v_a$ . Then apply KCL at node b to find  $i_m$ .

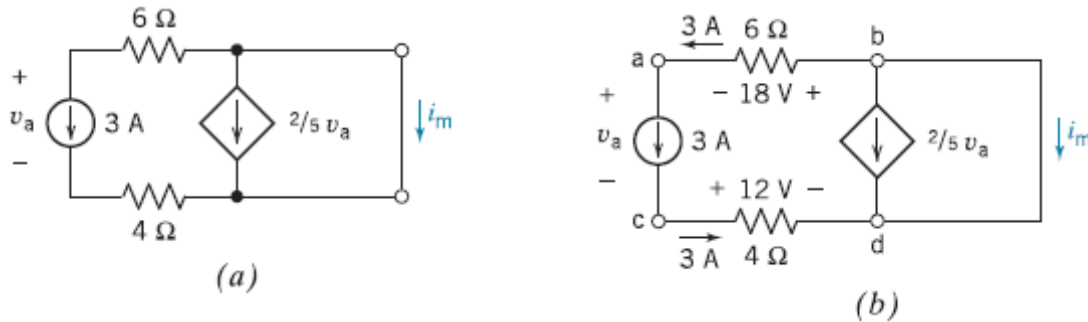


Figure P 3.2-18

**Solution:**

$$-18 + 0 - 12 - v_a = 0 \Rightarrow v_a = -30\text{ V} \quad \text{and} \quad i_m = \frac{2}{5}v_a + 3 \Rightarrow i_m = 9\text{ A}$$

**P3.2-26** Consider the circuit shown in Figure P3.2-26. Determine the values of

(a) The current  $i_a$  in the  $20\text{-}\Omega$  resistor.

(b) The voltage  $v_b$  across the  $10\text{-}\Omega$  resistor.

(c) The current  $i_c$  in the independent voltage source.


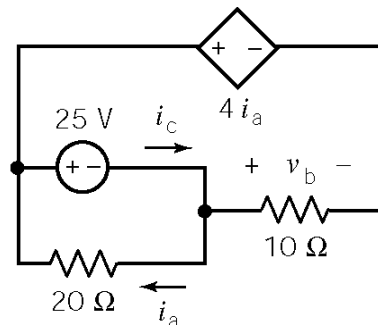


Figure P3.2-26

**Solution:**

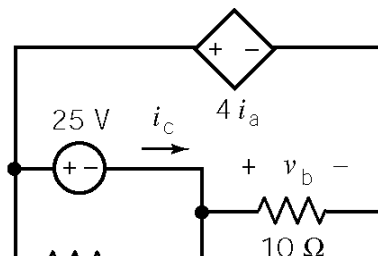

**P3.2-28** Consider the circuit shown in Figure 3.2-28.


a. Determine the value of the power supplied by each independent source.

b. Determine the value of the power received by each resistor.

c. Is power conserved?

**Solution:**

Apply KCL twice and KVL to get

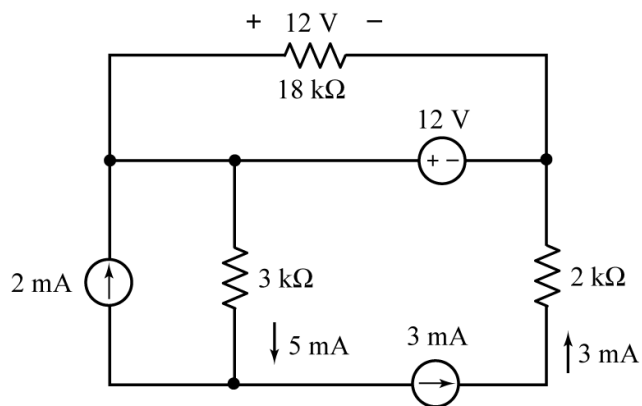

Apply Ohm's law 3 times to get

Note: The 2/3 mA below should be flipped to →


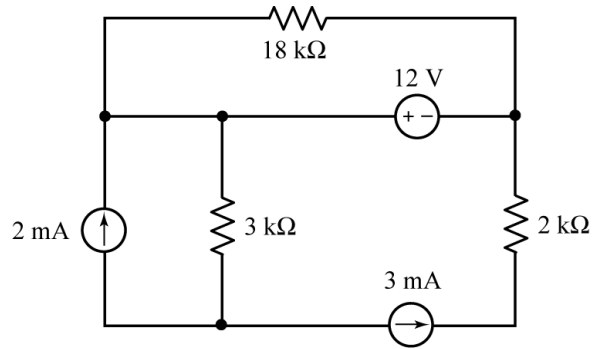
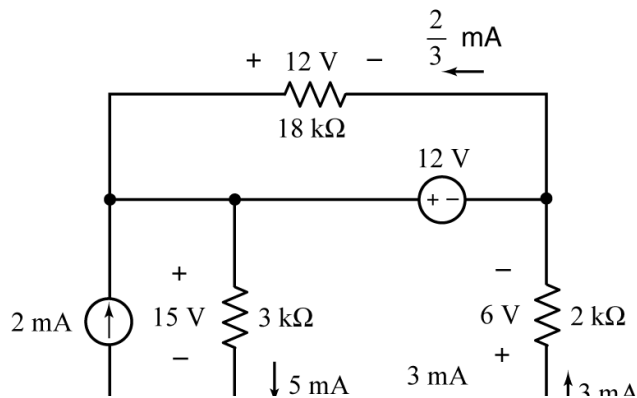


Figure 3.2-28

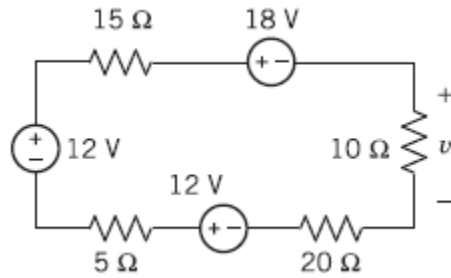**P 3.3-7** Determine the value of voltage  $v$  in the circuit shown in Figure P 3.3-7.



**Solution:**


All the elements are connected in series.

Replace the series voltage sources with a single equivalent voltage having voltage

$$12 + 12 - 18 = 6 \text{ V.}$$

Replace the series  $15 \Omega$ ,  $5 \Omega$  and  $20 \Omega$  resistors by a single equivalent resistance of


$$15 + 5 + 20 = 40 \Omega.$$

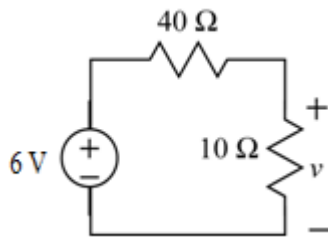

By voltage division

$$v = \left( \frac{10}{10 + 40} \right) 6 = \frac{6}{5} = 1.2 \text{ V}$$


**P 3.4-8** Determine the value of the voltage  $v$  in Figure P 3.4-8.

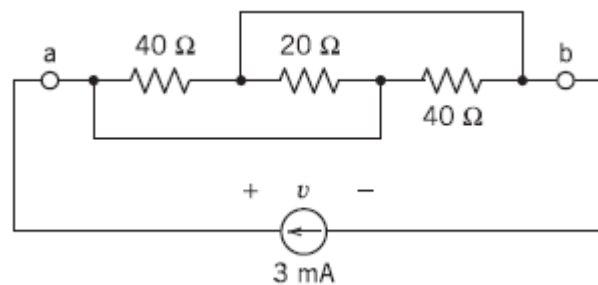

**Figure P 3.4-8**

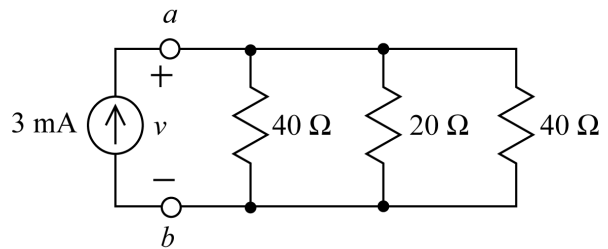**Solution:**

Each of the resistors is connected between nodes  $a$  and  $b$ . The resistors are connected in parallel and the circuit can be redrawn like this:




Then

$$40 \parallel 20 \parallel 40 = 10\Omega$$

so

$$v = 10(0.003) = 0.03 = 30\text{ mV}$$

**P 3.4-9** Determine the power supplied by the dependent source in Figure P 3.4-9.

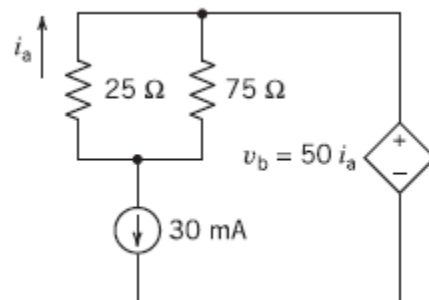

**Figure P 3.4-9**

**Solution:**


Use current division to get

$$i_a = -\frac{75}{25+75}(30 \times 10^{-3}) = -22.5 \text{ mA}$$


so 
$$v_b = 50(-22.5 \times 10^{-3}) = -1.125 \text{ V}$$

The power supplied by the dependent source is given by
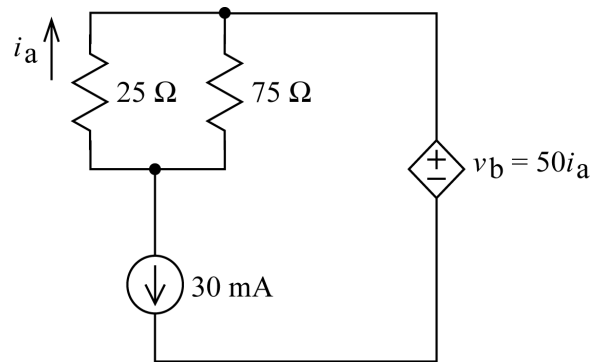
$$p = -(30 \times 10^{-3})(-1.125) = 33.75 \text{ mW}$$



**P 3.4-10** Determine the values of the resistances  $R_1$  and  $R_2$  for the circuit shown in Figure P 3.4-10.

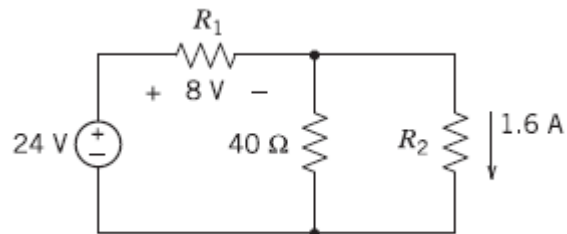

**Figure P 3.4-10**

**Solution:**

Using voltage division

$$8 = \frac{R_1}{R_1 + \frac{40R_2}{R_2 + 40}} \times 24 \quad \Rightarrow \quad \frac{1}{3} = \frac{R_1(R_2 + 40)}{R_1R_2 + 40(R_1 + R_2)}$$

$$\Rightarrow R_1R_2 + 40(R_1 + R_2) = 3R_1R_2 + 120R_1 \quad \Rightarrow \quad R_1 = \frac{40R_2}{2R_2 + 80}$$

Using KVL


$$24 = 8 + R_2(1.6) \quad \Rightarrow \quad R_2 = 10 \, \Omega$$

Then

$$R_1 = \frac{40(10)}{2(10) + 80} = 4 \, \Omega$$



**P 3.5-2** Determine the power supplied by each source in the circuit shown in Figure P 3.5-2.

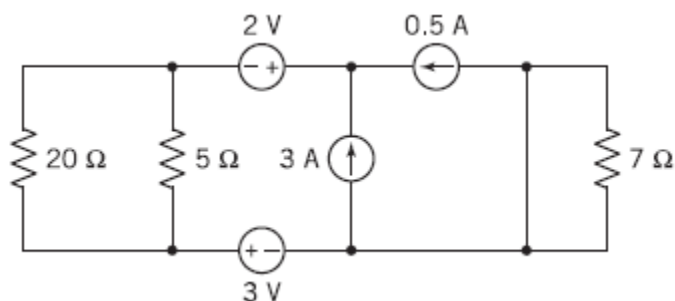

**Figure P 3.5-2**


**Solution:**

The 20-Ω and 5-Ω resistors are connected in parallel. The equivalent resistance is  $\frac{20 \times 5}{20 + 5} = 4 \, \Omega$ . The 7-Ω resistor is connected in parallel with a short circuit, a 0-Ω resistor. The equivalent resistance is


$\frac{0 \times 7}{0 + 7} = 0 \, \Omega$ , a short circuit.

The voltage sources are connected in series and can be replaced by a single equivalent voltage source.

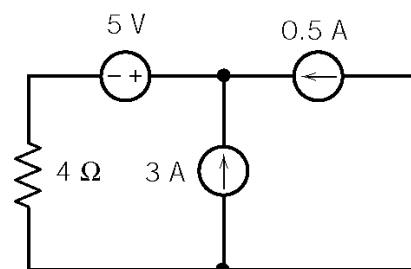After doing so, and labeling the resistor currents, we have the circuit shown.



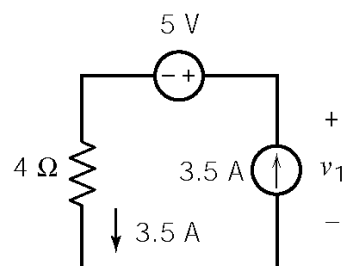The parallel current sources can be replaced by an equivalent current source.




Apply KVL to get

$$-5 + v_1 - 4(3.5) = 0 \Rightarrow v_1 = 19 \, \text{V}$$

The power supplied by each sources is:

Source	Power delivered
8-V voltage source	$-2(3.5) = -7 \text{ W}$
3-V voltage source	$-3(3.5) = -10.5 \text{ W}$
3-A current source	$3 \times 19 = 57 \text{ W}$
0.5-A current source	$0.5 \times 19 = 9.5 \text{ W}$


**P 3.6-3** Find  $i$  using appropriate circuit reductions and the current divider principle for the circuit of Figure P 3.6-3.

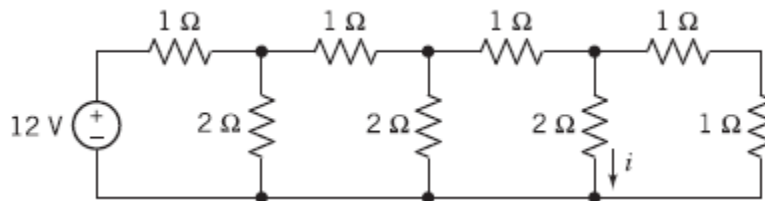


**Figure P 3.6-3**

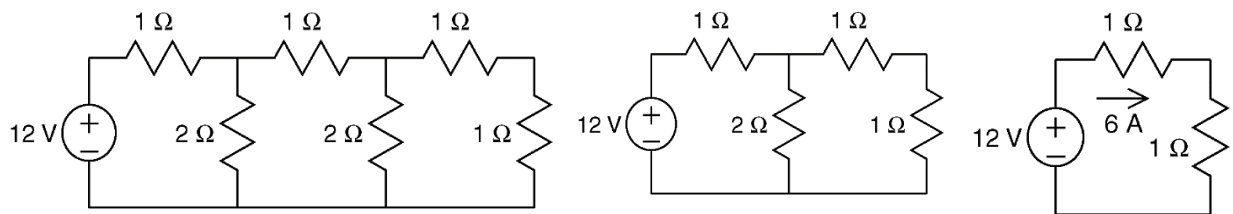**Solution:**


Reduce the circuit from the right side by repeatedly replacing series  $1 \Omega$  resistors in parallel with a  $2 \Omega$  resistor by the equivalent  $1 \Omega$  resistor



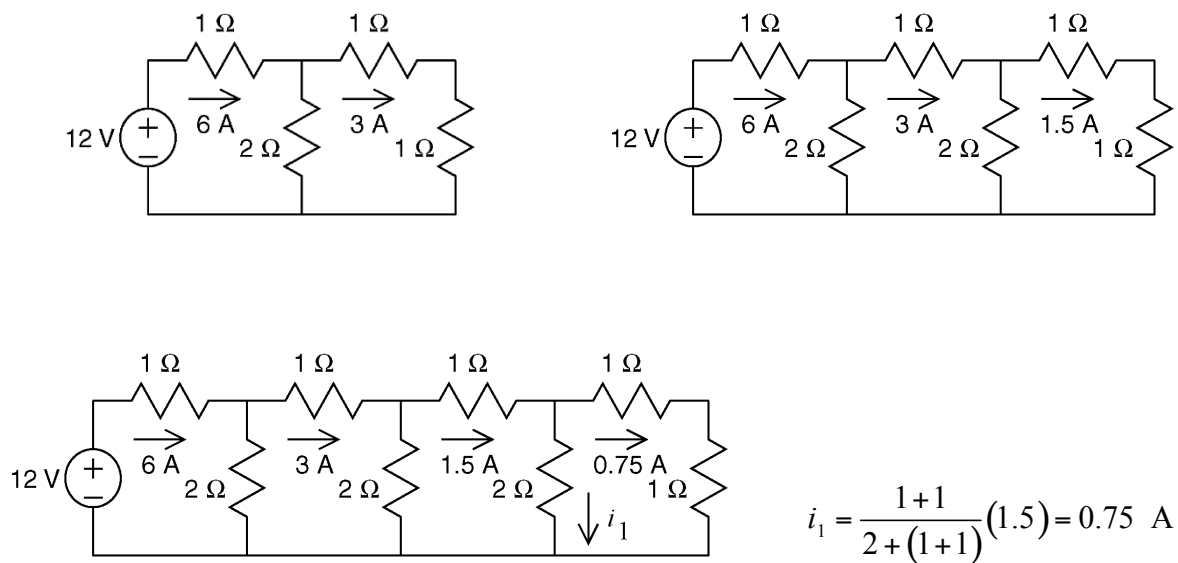This circuit has become small enough to be easily analyzed. The vertical  $1 \Omega$  resistor is equivalent to a  $2 \Omega$  resistor connected in parallel with series  $1 \Omega$  resistor:



**P 3.6-20** Determine the values of  $i$ ,  $v$ , and  $R_{eq}$  by the circuit model shown in Figure P 3.6-20, given that  $v_{ab} = 18 \text{ V}$ .

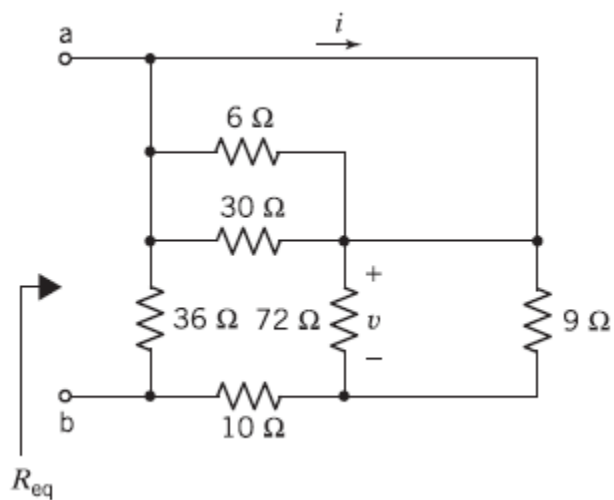


**Figure P 3.6-20**

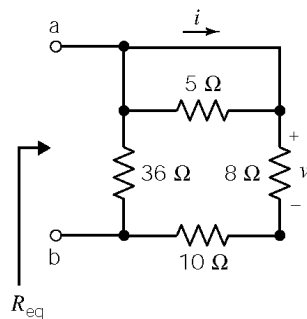**Solution:**

Replace parallel resistors by equivalent resistors:

$$6 \parallel 30 = 5 \Omega \text{ and } 72 \parallel 9 = 8 \Omega$$




A short circuit in parallel with a resistor is equivalent to a short circuit.

$$R_{eq} = 36 \parallel (8 + 10) = 12 \, \Omega$$

Using voltage division when  $v_{ab} = 18 \, \text{V}$ :

$$v = \frac{8}{8+10} v_{ab} = \frac{4}{9}(18) = 8 \, \text{V}$$

$$i = \frac{v}{8} = 1 \, \text{A}$$

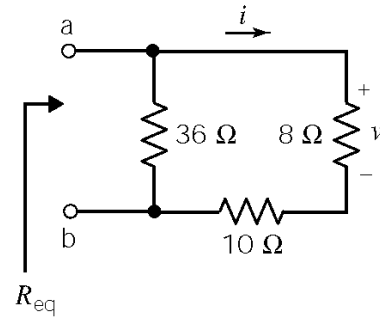

**P 3.6-21** Determine the value of the resistance  $R$  in the circuit shown in Figure P 3.6-22, given that  $R_{eq} = 9 \, \Omega$ .

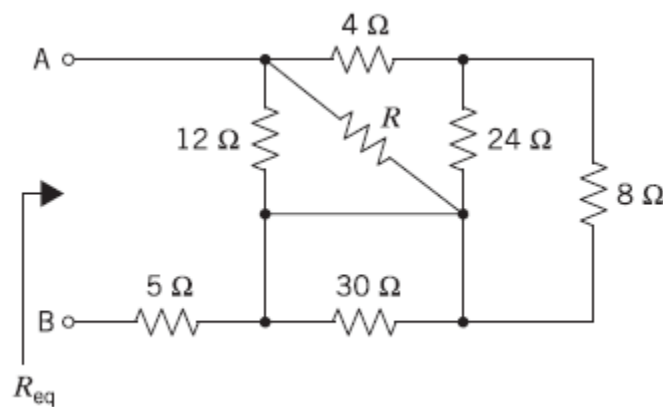


Figure P 3.6-22

### Solution:

Replace parallel resistors by an equivalent resistor:

$$8 \parallel 24 = 6 \Omega$$

A short circuit in parallel with a resistor is equivalent to a short circuit.



Replace series resistors by an equivalent resistor:

$$4 + 6 = 10 \Omega$$

Now

$$9 = R_{eq} = 5 + (12 \parallel R \parallel 10)$$
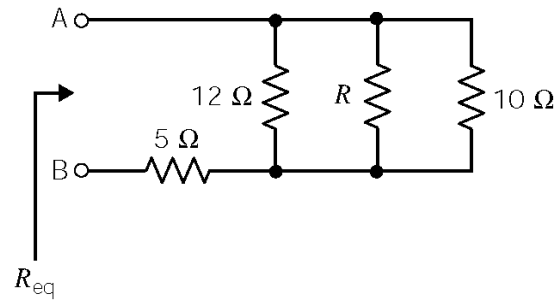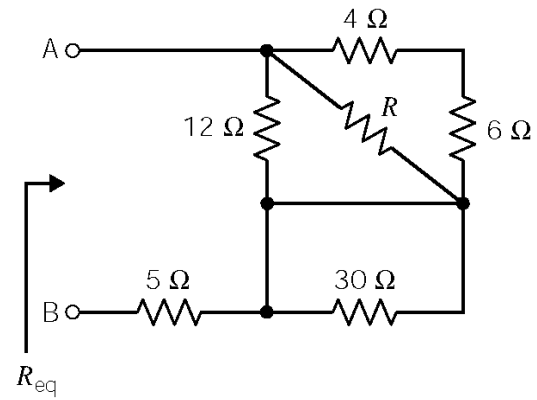
$$4 = \frac{R \times \frac{60}{11}}{R + \frac{60}{11}} \Rightarrow R = 15 \Omega$$



**P 3.6-28** Determine the value of the resistance  $R$  that causes the voltage measured by the voltmeter in the circuit shown in Figure P 3.6-28 to be 6 V.

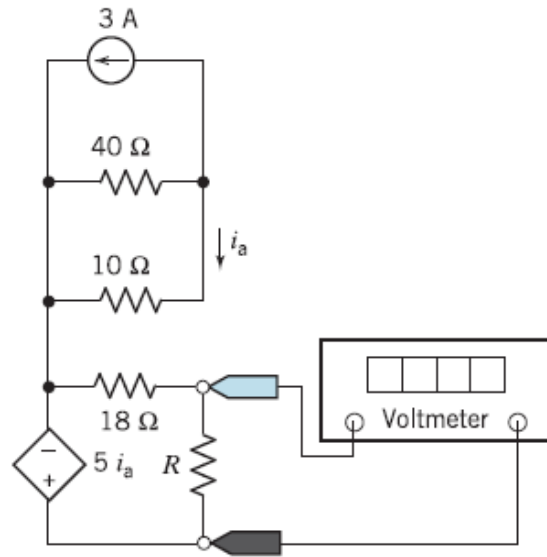


Figure P 3.6-28

**Solution:**

Use current division in the top part of the circuit to get

$$i_a = \left( \frac{40}{40 + 10} \right) (-3) = -2.4 \text{ A}$$

Next, denote the voltage measured by the voltmeter as  $v_m$  and use voltage division in the bottom part of the circuit to get

$$v_m = \left( \frac{R}{18 + R} \right) (-5 i_a) = \left( \frac{-5 R}{18 + R} \right) i_a$$


Combining these equations gives:

$$v_m = \left( \frac{-5 R}{18 + R} \right) (-2.4) = \frac{12 R}{18 + R}$$

When  $v_m = 6 \text{ V}$ ,

$$6 = \frac{12 R}{18 + R} \Rightarrow R = \frac{6 \times 18}{12 - 6} = 18 \text{ } \Omega$$


**P3.6-47** Determine the values of the voltages,  $v_1$  and  $v_2$ , and of the current,  $i_3$ , in the circuit shown in Figure P3.6-47.

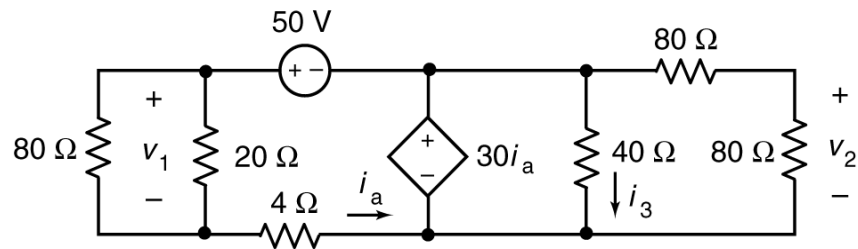

**Figure P3.6-47**

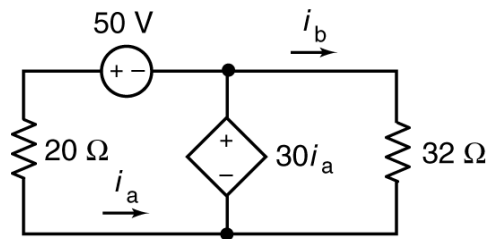**Solution:**

Replace series and parallel combinations of resistors by equivalent resistors to get




( $4 + (80 \parallel 20) = 4 + 16 = 20 \, \Omega$  and  $40 \parallel (80 + 80) = 40 \parallel 160 = 32 \, \Omega$ .) Next, apply KVL to the left mesh to get

$$50 + 30i_a - 20i_a = 0 \Rightarrow i_a = \frac{50}{20 - 10} = -5 \, \text{A} \quad \text{and} \quad 30i_a = -150 \, \text{V}$$

$$i_b = \frac{30i_a}{32} = \frac{-150}{32} = -4.6875 \, \text{A}$$

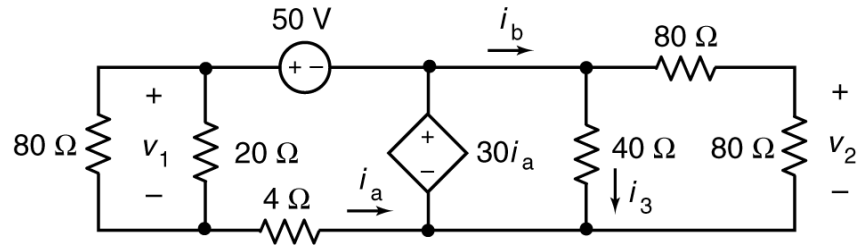Ohm's law gives  
Label  $i_b$  on the original circuit



Finally

$$v_1 = (80 \parallel 20)i_a = 16(-5) = -80\text{ V}, \quad v_2 = \frac{1}{2}(30i_a) = -75\text{ V}$$

and

$$i_3 = \frac{80 + 80}{40 + (80 + 80)}i_b = \frac{4}{5}(-4.6875) = -3.75\text{ A}$$